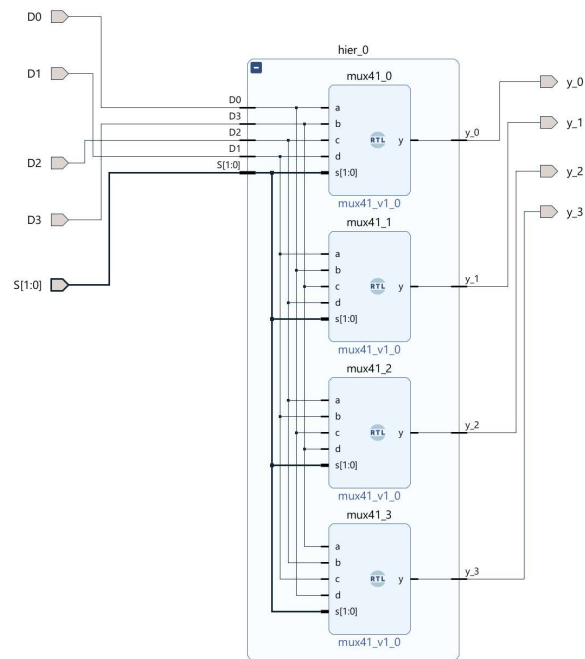


Assignment 19: Design 4-bit Barrel Shifter using 4:1 Mux.

Block Diagram



Simulation

