

Assignment 32: Design a PAL Circuit

Implement the SOP equation mentioned in the instruction in Live Circuit Simulator.

PAL circuit for the equation $A*B' + A'*B$

