
Assignment 20: Design 8:1 Mux using 4:1 Mux.

Block Diagram

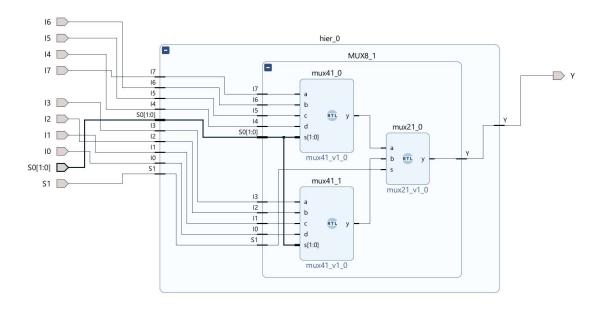

Simulation

