

## Assignment 28: Implement 4-bit Down counter with Reset and Load Control pin

- 1) When user apply active high to reset counter output must be 4'b0000
- 2) Counter should work when Reset is having value of Active Low
- 3) When user apply active high to load it should start counting from the user loaded value
- 4) If user have not loaded any value then it should start counting from 0

Code:

```
1  `timescale 1ns / 1ps
2
3  module counter(
4      input rst, clk, ld, [3:0] ldvalue,
5      output [3:0] res);
6
7      reg [3:0] temp;
8
9      always@(posedge clk or posedge rst) begin
10         if(rst == 1'b1)
11             begin
12                 temp <= 4'b0000;
13             end
14         else
15             begin
16                 if (ld == 1'b1)
17                     temp <= ldvalue;
18                 else
19                     begin
20                         temp <= temp - 1'b1;
21                     end
22             end
23         end
24
25     assign res = temp;
26
27 endmodule
28
```

Simulation:

