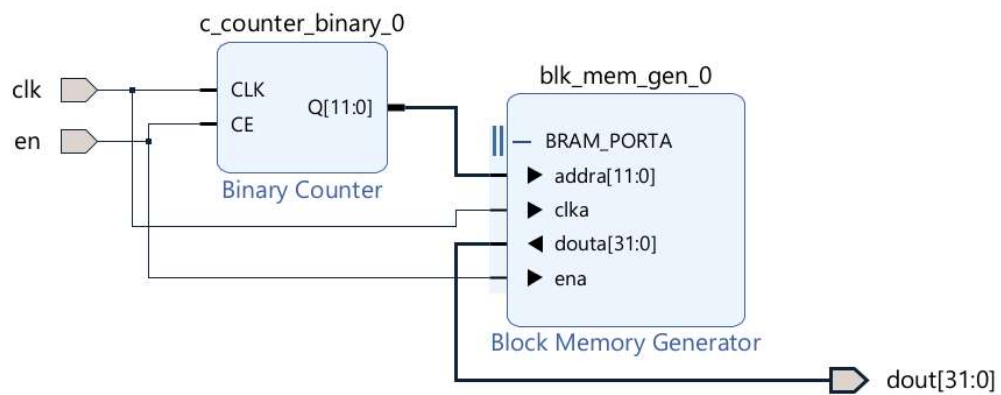


## Assignment 23: Create Modulated Sinc signal using Single Port ROM

### Block Diagram



### Behavioral Simulation

